



**Stellenbosch**

UNIVERSITY  
IYUNIVESITHI  
UNIVERSITEIT

# **E344 Assignment 1**

Gary Allen

23905093

Report submitted in partial fulfilment of the requirements of the module  
Design (E) 344 for the degree Baccalaureus in Engineering in the Department of Electrical  
and Electronic Engineering at Stellenbosch University.

August 1, 2022

## Plagiaatverklaring / *Plagiarism Declaration*

1. Plagiaat is die oorneem en gebruik van die idees, materiaal en ander intellektuele eiendom van ander persone asof dit jou eie werk is.

*Plagiarism is the use of ideas, material and other intellectual property of another's work and to present it as my own.*

2. Ek erken dat die pleeg van plagiaat 'n strafbare oortreding is aangesien dit 'n vorm van diefstal is.

*I agree that plagiarism is a punishable offence because it constitutes theft.*

3. Ek verstaan ook dat direkte vertalings plagiaat is.


*I also understand that direct translations are plagiarism.*

4. Dienooreenkomstig is alle aanhalings en bydraes vanuit enige bron (ingesluit die internet) volledig verwys (erken). Ek erken dat die woordelike aanhaal van teks sonder aanhalingstekens (selfs al word die bron volledig erken) plagiaat is.

*Accordingly all quotations and contributions from any source whatsoever (including the internet) have been cited fully. I understand that the reproduction of text without quotation marks (even when the source is cited) is plagiarism*

5. Ek verklaar dat die werk in hierdie skryfstuk vervat, behalwe waar anders aangedui, my eie oorspronklike werk is en dat ek dit nie vantevore in die geheel of gedeeltelik ingehandig het vir bepunting in hierdie module/werkstuk of 'n ander module/werkstuk nie.

*I declare that the work contained in this assignment, except where otherwise stated, is my original work and that I have not previously (in its entirety or in part) submitted it for grading in this module/assignment or another module/assignment.*

23905093	
Studentenommer / <i>Student number</i>	Handtekening / <i>Signature</i>
G. Allen	August 1, 2022
Voorletters en van / <i>Initials and surname</i>	Datum / <i>Date</i>

# Contents

<b>Declaration</b>	<b>i</b>
<b>List of Figures</b>	<b>iii</b>
<b>Nomenclature</b>	<b>iv</b>
<b>1. Literature review</b>	<b>1</b>
1.1. Operational amplifiers . . . . .	1
1.2. Current sensing . . . . .	3
<b>2. Detail design</b>	<b>4</b>
2.1. Current sensor . . . . .	4
<b>3. Results</b>	<b>6</b>
3.1. Current sensor . . . . .	6
3.1.1. Simulation . . . . .	6
3.1.2. Implementation . . . . .	7
<b>4. Physical implementation</b>	<b>8</b>
<b>Bibliography</b>	<b>9</b>
<b>A. Social contract</b>	<b>10</b>
<b>B. GitHub Activity Heatmap</b>	<b>11</b>

# List of Figures

1.1. Non-inverting amplifier [3]	2
1.2. Differential amplifier [3]	2
1.3. Instrumentation amplifier [3]	2
1.4. Modified non-inverting amplifier [4]	2
1.5. Illustration of Hall Effect Sensors	3
2.1. Circuit diagram of final configuration	5
3.1. Amplifier output in response to step input	6
3.2. Current draw of op-amp	6
3.3. Amplifier noise rejection	7
3.4. Amplifier response time	7
4.1. Final Circuit Implementation	8

# Nomenclature

## Variables and functions

$V_{ss}$	Voltage positive.
$V_{dd}$	Voltage negative.

## Acronyms and abbreviations

CMRR	Common Mode Rejection Ratio
RC	Resistor Capacitor

# Chapter 1

## Literature review

The following study presents an overview of the current configurations and design techniques for both operational amplifier and current-sensing circuits. Operational amplifier limitations are considered, as well as the system requirements. These findings are then discussed to ensure that there is enough information to aid the design process.

### 1.1. Operational amplifiers

#### Limitations

Often, it is applicable to design an amplifier using the ideal operational amplifier model, however this may be inadequate in low voltage, high current or high frequency environments. The following are common limitations of non-ideal op-amps [1]:

- Voltage supply saturation. For given  $k$ , output cannot go above  $V_{ss} - k$  or below  $V_{dd} + k$ .
- Finite bandwidth. Output signal magnitude reduces at high frequencies. This effect can be catered for using the gain-bandwidth product equation.
- Offset voltage/bias current. Even with no input, there exists a small "offset voltage" and "bias current" into the amplifier. This results in unwanted voltage at the output.
- Finite slew rate. The output cannot change quicker than a specific rate. This is different to the high-cutoff, but has a similar limiting effect.
- Finite common-mode rejection ratio (CMRR). An op-amp should only amplify  $V_+ - V_-$ , but also amplifies the unwanted common signal (e.g. noise) on both inputs.

#### Considerations

System requirements should first be considered in order to attain an overview of the specifications:

- The output range of the circuit should be from 0.1 to 3 V. Since a low-side current sense resistor will be used, this means initial measurements will be at a lower voltage initially.
- The step response of the circuit should reach 90% of its output in less than 100 ms. The op-amp's slew rate should be analyzed to ensure this condition is met.

- Noise above 1 kHz should be filtered out such that a 10 mV, 1 kHz signal at the input is less than 250 mV at the output. Filter options should therefore be researched.

It is clear that voltage supply saturation, slew rate and CMRR are the main parameters to be considered. A filter circuit should also be designed for noise specifications.

## MCP6242


The op-amp used in this project is the MCP6242. Listed below are its notable parameters [2]:

- Typical CMMR of 75 dB (DC) to 65 dB (1 kHz).
- Ability to output between 0.035 and 5.465 V if  $V_{ss} = 6$  V and  $V_{dd} = 0$  V
- Slew rate of 0.3 V/uS.


## Configurations

A number of well-known op-amp configurations exist that all achieve slightly different amplification goals. The following list compares common configurations [3] which may achieve this project's goal of amplifying a small-signal voltage across a resistor. The figures below also include a modified non-inverting amplifier to allow for input signal filtering:


Type	Advantages	Disadvantages
Non-inverting	<ul style="list-style-type: none"> <li>- Simple to design and build</li> <li>- High input impedance</li> </ul>	<ul style="list-style-type: none"> <li>- Large input bias currents</li> <li>- Amplifies noise from input</li> </ul>
Differential	<ul style="list-style-type: none"> <li>- Good noise rejection</li> <li>- Flexible</li> </ul>	<ul style="list-style-type: none"> <li>- Complex design</li> <li>- Low input impedance</li> </ul>
Instrumentation	<ul style="list-style-type: none"> <li>- Same as differential</li> <li>- Very high input impedance</li> </ul>	<ul style="list-style-type: none"> <li>- Complex and expensive design</li> </ul>

 


**Figure 1.1:**  
Non-inverting  
amplifier [3]

 

**Figure 1.2:** Dif-  
ferential ampli-  
fier [3]

 

**Figure 1.3:** In-  
strumentation  
amplifier [3]

 


**Figure 1.4:**  
Modified  
non-inverting  
amplifier [4]

## 1.2. Current sensing

### Sensing Techniques

Measurement techniques are usually either "invasive" or "non-invasive". Invasive techniques tap into the circuit directly and often have a significant affect on its operation, whereas non-invasive techniques might use e.g. the circuit's magnetic flux to determine the strength of the current. A list of a few of these techniques [5] include:

- A current-sensing resistor in series, which uses Ohm's law with a voltage measurement to calculate current.
- Hall element sensors, which determine the strength of current based on how much its magnetic field "bends" another current left and right (which creates a potential difference).
- Coil techniques, which make using of Faraday's law.

 

**Figure 1.5:** Illustration of Hall Effect Sensors

### High-side vs low-side sensing

These names of these two techniques refer to the placement of a current-sense resistor relative to the load. For circuits which draw higher currents, high-side sensing can be used (placing the resistor closer to the positive of the voltage source) and is often more convenient. Low-side sensing, on the other hand, can potentially cause ground loop issues [6], but has the ability to detect faults earlier.

### AC, DC, and Power Requirements

As mentioned, there are various non-invasive and even wireless techniques used to measure current. Faraday's law is used to make measurements using induction, which requires AC. The Hall effect and sense resistors, on the other hand, are often used in the DC case. Wireless techniques have benefits over resistors in that they can be configured to draw much less power, whereas sense resistors usually need high power handling capabilities as they pass through all current drawn by the actual load.



# Chapter 2

## Detail design

The following process details the design and calculations for the current sensor circuit. It provides insight into what decisions were made, as well as the justifications behind them.

### 2.1. Current sensor

#### Configuration

The differential amplifier configuration will be used for this project for the following reasons:

- The configuration is specifically designed to reject common-mode noise, which the non-inverting amp suffers from.
- Only 1 op-amp is needed.
- The design is relatively simple compared to the instrumentation amplifier.

However, a modified version with two extra capacitors will be used. Two capacitors will be added in parallel with  $R_f$  and  $R_g$  called  $C_f$  and  $C_g$  respectively. It is important that these capacitors have the same value in order to preserve CMRR [3]. It is likely, however, that one of these will be dominant due to differing resistor values, and therefore this design will only consider the filter to be first-order. This is acceptable, however, due to the amplifier's noise-rejecting capabilities.

#### Gain and Cutoff

Before calculating component values, both the cutoff frequency of the RC filter, and the DC gain of the amplifier, need to be determined. The gain of the amplifier should be determined such that, when the maximum current flows through the sense resistor, the maximum voltage is output.

First, the maximum current of the motor should be measured. This can be done by connecting the motor to a power supply (through an ammeter), stalling the motor, and reading the output current. With a supply voltage of 6.4 V connected, the motor for this project read 740 mA, however different motors may read between 1 and 1.5 A. The average running current, however, is between 200 mA and 300 mA. A value of  $I_{max} = 1A$  will therefore be chosen to allow for more headroom and a slightly lower gain. Since a sense resistor of  $10\text{ m}\Omega$  is to be used, the maximum voltage through this resistor will therefore be 8 mV. A

gain of  $\frac{3V}{10mV} = 300$  is therefore chosen. Although this voltage level is small, it is expected, given that the resistance value is so small. It is also desirable, as it shows that the circuit is not "stealing" too much power from the motor itself.


The cutoff frequency  $f_H$  should be selected such that the slew rate requirements are not affected, while still adequately filtering a 1 kHz noise signal. In order for the noise requirement to be satisfied, the input signal must be attenuated by  $20 \log \frac{300 \cdot 10mV}{250mV} \approx 22dB$ . This means the cutoff should be around 100 Hz (a decade below 1 kHz). Since the specification requires a change from 0.1 to  $3 \times 0.9 = 2.7V$  in less than 100 ms, the output should be capable of oscillating at  $\frac{1}{50ms} = 20Hz$ , which is below the designed cutoff.

Since input current of the circuit needs to be limited below 150 uA, high resistor values should be chosen:

- Assuming  $i_n = 0$ , choose  $\frac{V_{out(max)}}{R_1 + R_f} \ll 150uA \therefore R_1 + R_f \gg 20k\Omega$ . Choose  $R_f = 100k\Omega$ .
- $G = \frac{R_f}{R_1} = 300 \therefore R_1 = 330\Omega$
- Choose  $R_2 = R_1 = 330\Omega$  and  $R_g = R_f = 100k\Omega$  for differential symmetry.
- Since  $R_{eq}$  of  $C_f$  is  $R_f$  and of  $C_g$  is  $R_g || R_2$ , it is clear that  $C_f$  is dominant,  $\therefore C_f = \frac{1}{2\pi \cdot R_f \cdot 100Hz} \approx 15nF$ . Also set  $C_g = 15nF$  for symmetry. It should be noted, however, that this technique (using time constants) is not always valid - especially in complex circuits such as these - and so these results should be checked using simulations.

## Circuit diagram

The following figure details the final circuit design for the sensor and amplifier system.

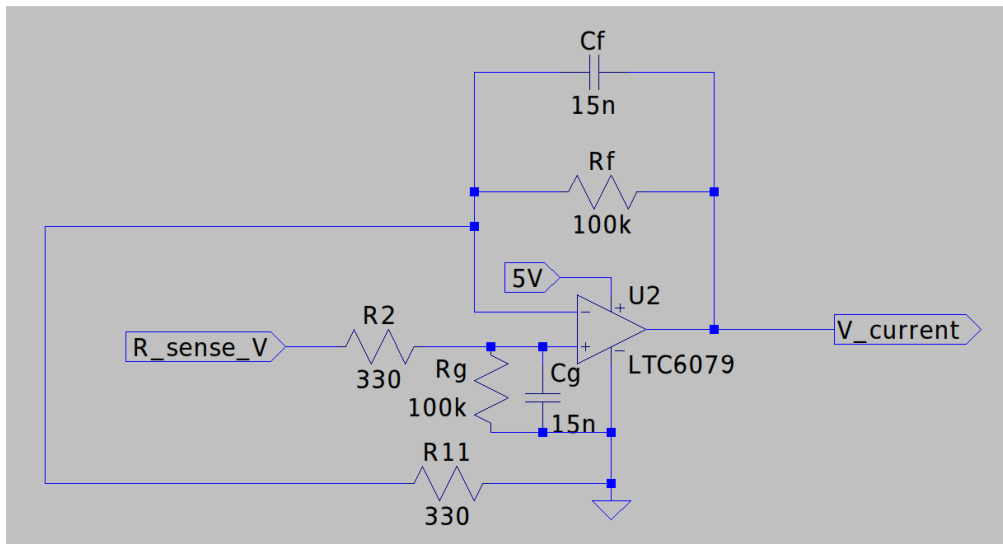

**Figure 2.1:** Circuit diagram of final configuration

A single 5 V supply will be used. Although there are benefits to a dual rail supply, that would prove impractical in the context of the larger system.


# Chapter 3

## Results


### 3.1. Current sensor

#### 3.1.1. Simulation

After running initial simulations, it was clear that the constant assumed in the design stage for the dominant capacitor  $C_f$  was too high. The capacitor value was then experimentally increased to 100nF where a satisfactory response which was reasonably below 250 mV (10-20%) was obtained. This section details the rest of the results of these simulations.

 

**Figure 3.1:** Amplifier output in response to step input

 

**Figure 3.2:** Current draw of op-amp

As can be seen, all specifications were adhered to:

- The noise level at idle is well below the 250 mV requirement.
- The step response input changes 20-25 ms, which is below the 100 ms requirement.
- The power draw of the circuit (as measure at the positive terminal of the op-amp) is less than 85 uA, which is much less than the specified 150 uA.


Lastly, the input simulation parameters were modified during testing to analyze the various output voltages for different input currents. For input currents of 400mA, 500mA, 800mA and 1A, the output voltages were 1.22V, 1.52, 2.43 and 3.024 V respectively. This matches perfectly with the initial design.

### 3.1.2. Implementation


Tests were conducted with a function generator to ensure the amplifier met specifications.

As can be seen in Figure 3.3, the amplifier noise requirement was satisfied. The input signal (channel 1, bottom) is a 10 mV<sub>pp</sub> 1 kHz sine wave with 6 mV offset. It is required that a sinusoidal "noise" signal greater than this frequency should not be amplified to more than 250 mV<sub>pp</sub>. An output of 1.13 V - 0.949 V = 181 mV was obtained - within the threshold.

In Figure 3.4, the amplifier's step response time was recorded as 4.957 ms, which is much below the 100 ms requirement. This time is 4x better than the designed circuit, presumably due to the increased resistance value and other tolerances.

 

**Figure 3.3:** Amplifier noise rejection

 

**Figure 3.4:** Amplifier response time

Current measurements were then made with the motor connected, as visible in Table 3.1. As can be analyzed, there is an offset voltage of 0.42 V at the output. The actual gain can be calculated as e.g.  $\frac{1.42\text{ V} - 0.42\text{ V}}{210\text{ mA} \cdot 10\text{ m}\Omega} = 476\text{ V/V}$ . With the new resistor, an ideal gain of  $\frac{120\text{ k}\Omega}{330\text{ k}\Omega} = 363.6\text{ V/V}$  was expected, however due to the nature of the circuit (which contains 4 resistors) a tolerance of 10% \* 4 should be accounted for, which explains the higher gain.

Motor Condition	PSU Current (mA)	Output Voltage (V)
Stall	1200	3.31
Slight Load	305	1.96
Free Running	210	1.42
I = 150 mA	150	1.13
I = 100 mA	100	0.91
I = 50 mA	50	0.63
I = 0 mA	0	0.42


**Table 3.1:** Measurements of Motor Current vs Voltage

# Chapter 4

## Physical implementation

The implementation of the circuit was different in two ways compared to the original design:

- 120 k $\Omega$  resistors were used instead of 100 k $\Omega$ , as they were easier to obtain, and would only result in a slightly larger gain and lower cutoff.
- The amplifier circuit was powered with regulated 3.3 V. This was done to protect the ESP's input pins by saturating the output when it would have been too large.

 

**Figure 4.1:** Final Circuit Implementation

# Bibliography

- [1] Tutorials Point, “Physical limitations of operational amplifiers.” [Online]. Available: <https://www.tutorialspoint.com/physical-limitations-of-operational-amplifiers>
- [2] Microchip, “Mcp6241/1r/1u/2/4.” [Online]. Available: <https://www.tutorialspoint.com/physical-limitations-of-operational-amplifiers>
- [3] WikiBooks, “Op amp configurations.” [Online]. Available: <https://ww1.microchip.com/downloads/aemDocuments/documents/OTH/ProductDocuments/DataSheets/21882d.pdf>
- [4] ElectronicsTutorials, “Second order filters.” [Online]. Available: <https://www.electronics-tutorials.ws/filter/second-order-filters.html>
- [5] HiokiUSA, “6 current sensing methods.” [Online]. Available: <https://hiokiusa.com/6-current-sensing-methods/>
- [6] AllAboutCircuits, “Low side vs high side sensing.” [Online]. Available: <https://www.allaboutcircuits.com/technical-articles/resistive-current-sensing-low-side-versus-high-side-sensing/>

# Appendix A

## Social contract



UNIVERSITEIT • STELLENBOSCH • UNIVERSITY  
jou kennisvenoot • your knowledge partner

### E-design 344 Social Contract

2022

The purpose of this document is to establish commitment between the student and the organisers of E344. Beyond the commitment made here, it is not binding.

In the months preceeding the term, the lecturer (Thinus Booysen) and a few paid helpers (Rita van der Walt, Keegan Hull, and Michael Ritchie) spent countless hours to prepare for E344 to ensure that you get your money's worth, that you are enabled to learn from the module, and demonstrate and be assessed on your skills. We commit to prepare the assignments, to set the assessments fairly, to be reasonably available, and to provide feedback and support as best and fast we can. We will work hard to give you the best opportunity to learn from and pass analogue electronic design E344.

I, Gary Allen ..... have registered for E344 of my own volition with the intention to learn of and be assessed on the principals of analogue electronic design. Despite the potential publication online of supplementary videos on specific topics, I acknowledge that I am expected to attend the scheduled lectures to make the most of these appointments and learning opportunities. Moreover, I realise I am expected to spend the additional requisite number of hours on E344 as specified in the yearbook.

I acknowledge that E344 is an important part of my journey to becoming a professional engineer, and that my conduct should be reflective thereof. This includes doing and submitting my own work, working hard, starting on time, and assimilating as much information as possible. It also includes showing respect towards the University's equipment, staff, and their time.

Prof. MJ (Thinus) Booysen

Student number: 23905093

MJ Booysen

Digitally signed by MJ  
Booyesen  
Date: 2022.07.02  
13:22:09 +02'00'

Signature: ..... Signature: Alan

Date: 1 July 2022 ..... Date: 25 / 07 / 2022

# Appendix B

## GitHuB Activity Heatmap

